



# Digital Logic Design & Computer Architecture Lab report

Third assignment

## **PREPARED FOR**

Miss. Talebpour

## **PREPARED BY**

Mohsen Karbalaei Amini, 98242128

Mohammad Mehdi Parchami, 400243084

April 17, 2023,



# Serialized output multiplier

## Implementation (Part a)

We constructed a generic **(extra point part)**  $n \times n$  bit multiplier, that outputs the result synchronous to the *clk* signal in a serialized manner. We also embedded a *start* signal which enables us to do multiple multiplications in one test bench.

Here you can see the code:

```
module shift_add_multiply #(parameter n=32)(multiplier,multiplicand,start,clk,out);

    input [n - 1:0] multiplier, multiplicand;
    input          start,clk;
    output         out;

    reg [7:0] bit = 0;
    reg          out;
    reg [n:0]    product;
    reg [n - 1:0] m;

    always @(posedge clk)begin
        if(start || bit >= n + n - 1) begin
            bit = 0;
            product[n:0] = 0;
            out = 0;
            m = multiplier;
        end
        else begin
            if(bit < n) begin
                if (m[0])
                    product = product + {1'b0 , multiplicand} ;
            end
            m = m >> 1;
            out = product[0];
            product = product >> 1;
            bit = bit + 1;
        end
    end
endmodule
```

On each positive edge of the *clk* , *out* signal represents the last bit of the product (which won't be changed in the reminding sums), and then shifts the product to the right to make room for the new operations.

## Test Bench (part b)

Code and simulation:

```
module shift_add_mul_tb;

    // Inputs
    reg [30:0] multiplier;
    reg [30:0] multiplicand;
    reg start;
    reg clk;

    // Outputs
    wire out;

    // Instantiate the Unit Under Test (UUT)
    shift_add_multiply uut (
        .multiplier(multiplier),
        .multiplicand(multiplicand),
        .start(start),
        .clk(clk),
        .out(out)
    );

    /*always
    begin
        clk <= !clk;
        #50;
    end
    */
    initial begin
        // Initialize Inputs
        multiplier = 31'd8;
        multiplicand = 31'd8;
        start = 1;
        clk = 0;

        // Wait 100 ns for global reset to finish
        #10;
        #10;
        clk = 1;


        #10;
        #10;
        clk = 0;

        start = 0;
        forever #(20) clk = ~clk;


    end

endmodule
```

 The multiplication of  $8 \times 8 = 64 = (7'b100\_0000)$



# Synthesize

 

# Design Summary

Design Overview

- Summary
- IOB Properties
- Module Level Utilization
- Timing Constraints
- Pinout Report
- Clock Report
- Static Timing

Errors and Warnings

- Parser Messages
- Synthesis Messages
- Translation Messages
- Map Messages
- Place and Route Messa...
- Timing Messages
- Bitgen Messages
- All Implementation Me...

Detailed Reports

- Synthesis Report

Design Properties

- Enable Message Filtering

Optional Design Summary Contents

- Show Clock Report
- Show Failing Constraints
- Show Warnings
- Show Errors

shift\_add\_multiply Project Status (04/10/2023 - 07:00:42)

Project File:	shift_add_mul.xise	Parser Errors:	No Errors
Module Name:	shift_add_multiply	Implementation State:	Placed and Routed
Target Device:	xc3s100e-5vq100	Errors:	No Errors
Product Version:	ISE 14.7	Warnings:	<a href="#">2 Warnings (2 new)</a>
Design Goal:	Balanced	Routing Results:	<a href="#">All Signals Completely Routed</a>
Design Strategy:	<a href="#">Xilinx Default (unlocked)</a>	Timing Constraints:	<a href="#">All Constraints Met</a>
Environment:	<a href="#">System Settings</a>	Final Timing Score:	0 ( <a href="#">Timing Report</a> )

Device Utilization Summary

Logic Utilization	Used	Available	Utilization	Note(s)
Number of Slice Flip Flops	71	1,920	3%	
Number of 4 input LUTs	101	1,920	5%	
Number of occupied Slices	55	960	5%	
Number of Slices containing only related logic	55	55	100%	
Number of Slices containing unrelated logic	0	55	0%	
Total Number of 4 input LUTs	108	1,920	5%	
Number used as logic	101			
Number used as a route-thru	7			
Number of bonded IOBs	65	66	98%	
Number of BUFGMUXs	1	24	4%	
Average Fanout of Non-Clock Nets	1.78			

Design Summaryshift\_add\_mul\_tb.vshift\_add\_multiply (RTL1)shift\_add\_multiply (Tech1)